

ESP32-CAM Project Documentation

Team Alpha

John Doe • Jane Smith • Project Lead

University of Technology / Awesome Company Inc.

May 21, 2025

Project Overview & Goals

Project Name

ESP32-CAM Interfacing and Application

Team Members

- John Doe - Hardware Integration
- Jane Smith - Software Development
- Project Lead - System Architecture

Key Objectives

- Successfully program the ESP32-CAM module.
- Implement basic image capture.
- Explore [Your Specific Objective Here, e.g., Web Streaming, Object Detection].

Logical Connections and Signals

Power Connections

- ESP32-CAM **VCC** (+5V Input) \longleftrightarrow ESP32-CAM-MB **5V** (Output)
- ESP32-CAM **3V3** (+3.3V Output/Input) \longleftrightarrow ESP32-CAM-MB **3V3** (Output)
- ESP32-CAM **GND** (Ground) \longleftrightarrow ESP32-CAM-MB **GND** (Ground)
(Two separate GND connections are typically made for stability)

Programming & Serial Communication (UART0)

Note: TX (Transmit) of one device connects to RX (Receive) of the other.

- ESP32-CAM **IO1** (U0TXD - Default UART0 Transmit) \longrightarrow ESP32-CAM-MB **RXD** (Programmer Receive)
- ESP32-CAM **IO3** (U0RXD - Default UART0 Receive) \longleftarrow ESP32-CAM-MB **TXD** (Programmer Transmit)

Alternatively, using explicitly labeled UART pins on some ESP32-CAM

ESP32-CAM to ESP32-CAM-MB Pinout Summary

Wire Color (from Diagram)	ESP32-CAM Pin	ESP32-CAM-MB Pin
Yellow	3V3 (+3.3V Power)	3V3 (+3.3V Power Out)
Purple	IO1 (U0TXD / TX)	RXD (Programmer UART RX)
Dark Blue	IO3 (U0RXD / RX)	TXD (Programmer UART TX)
Sky Blue	GND (Ground)	GND (Ground)
Teal	VCC (+5V Power In)	5V (+5V Power Out)
Salmon	U0R (GPIO3 / Alt. RX)	TXD (Programmer UART TX)